

N1

$$\frac{V_1 - V_1}{R_1} = \frac{V_1 - V_2}{R_2} + C_2 \underbrace{\frac{d(V_0 - V_1)}{dt}}_{}$$

N2

$$\frac{V_1 - V_2}{R_2} = C_1 \frac{dV_2}{dt}$$

N3

$$\frac{V_0 - V_3}{R_4} = \frac{V_3 - 0}{R_3}$$

V1

Expandiendo C2

$$\frac{V_i - V_1}{R_1} = \frac{V_1 - V_2}{R_2} + C_2 \frac{dV_0}{dt} - C_2 \frac{dV_1}{dt}$$

V2 = V3

Despejando  $\dot{V}_1$

$$\frac{V_i}{R_1} - \frac{V_1}{R_1} = \frac{V_1}{R_2} - \frac{V_2}{R_2} + C_2 \frac{dV_0}{dt} - C_2 \frac{dV_1}{dt} \rightarrow \frac{\dot{V}_1}{R_1} = \frac{V_1}{R_2} - \frac{V_2}{R_2} + C_2 \frac{dV_0}{dt} - C_2 \frac{dV_1}{dt} + \frac{V_1}{R_1}$$

$$\rightarrow V_i = \frac{R_1}{R_2} V_1 - \frac{R_1}{R_2} V_2 + R_1 C_2 \frac{dV_0}{dt} - R_1 C_2 \frac{dV_1}{dt} + V_1$$

Despejando V3 de N3

$$\frac{V_0}{R_4} - \frac{V_3}{R_4} = \frac{V_3}{R_3}$$

$$\left( \frac{V_0}{R_4} = \frac{V_3}{R_3} + \frac{V_3}{R_4} \right) R_4 R_3$$

$$R_3 V_0 = V_3 R_4 + V_3 R_3$$

$$R_3 V_0 = (R_4 + R_3) V_3$$

$$\rightarrow \frac{R_3}{(R_4 + R_3)} V_0 = V_3$$

$$\dot{V}_3 = \frac{R_3}{(R_4 + R_3)} \frac{dV_0}{dt}$$

$$V_3 = V_2 \rightarrow \text{Por el op ideal}$$

Despejando V1 de N2

$$\frac{V_1}{R_2} - \frac{V_2}{R_2} = C_1 \frac{dV_2}{dt}$$

$$\left( \frac{V_1}{R_2} = C_1 \frac{dV_2}{dt} + \frac{V_2}{R_2} \right) R_2$$

$$V_1 = C_1 R_2 \frac{dV_2}{dt} + V_2$$

Sustituyendo V3 en V2

$$V_1 = C_1 R_2 \left( \frac{R_3}{(R_4 + R_3)} \frac{dV_0}{dt} \right) + \frac{R_3}{(R_4 + R_3)} V_0$$

$$\dot{V}_1 = C_1 R_2 \left( \frac{R_3}{(R_4 + R_3)} \frac{d^2 V_0}{dt^2} \right) + \frac{R_3}{(R_4 + R_3)} \frac{dV_0}{dt}$$

Sustituyendo  $V_1$  en  $V_i$

$$V_i = \frac{R_1}{R_2} \left[ C_1 R_2 \left( \frac{R_3}{(R_4+R_3)} \frac{dV_o}{dt} \right) + \frac{R_3}{(R_4+R_3)} V_o \right] - \frac{R_1}{R_2} \left( \frac{R_3}{(R_4+R_3)} V_o \right)$$

$$+ R_1 C_2 \frac{dV_o}{dt} - R_1 C_2 \left[ C_1 R_2 \left( \frac{R_3}{(R_4+R_3)} \frac{d^2 V_o}{dt^2} \right) + \frac{R_3}{(R_4+R_3)} \frac{dV_o}{dt} \right]$$

$$+ C_1 R_2 \left( \frac{R_3}{(R_4+R_3)} \frac{dV_o}{dt} \right) + \frac{R_3}{(R_4+R_3)} V_o$$

Agrupando términos

$$V_i = R_1 C_1 \left( \frac{R_3}{(R_4+R_3)} \frac{dV_o}{dt} \right) + \frac{R_1 R_3}{R_2 (R_4+R_3)} V_o - \frac{R_1 R_3}{R_2 (R_4+R_3)} V_o$$

$$+ R_1 C_2 \frac{dV_o}{dt} - R_1 C_2 C_1 R_2 \left( \frac{R_3}{R_4+R_3} \right) \frac{d^2 V_o}{dt^2} - \frac{R_1 C_2 R_3}{(R_4+R_3)} \frac{dV_o}{dt}$$

$$V_i = \underbrace{- \frac{R_1 R_2 R_3 C_1 C_2}{R_4+R_3} \frac{d^2 V_o}{dt^2}}_A + \underbrace{\frac{R_1 R_3 C_1}{R_4+R_3} \frac{dV_o}{dt}}_{\dot{V}_o} - \underbrace{\frac{R_1 R_3 C_2}{R_4+R_3} \frac{dV_o}{dt}}_{\dot{V}_o} + \underbrace{R_1 C_2 \frac{dV_o}{dt}}_{\dot{V}_o} + \underbrace{\frac{C_1 R_2 R_3}{R_4+R_3} \dot{V}_o}_{\ddot{V}_o} + \underbrace{\frac{C_1 R_3 R_2}{R_4+R_3} V_o}_{V_o}$$

$$X_1 = V_O \quad \dot{X}_1 = \ddot{V}_O$$

$$X_2 = \ddot{V}_O \quad \dot{X}_2 = \ddot{V}_O$$

$$\frac{1}{A} - A \ddot{V}_O = V_I - \frac{R_1 R_3 C_1}{R_4 + R_3} \ddot{V}_O + \frac{R_1 R_3 C_2}{R_4 + R_3} \ddot{V}_O - R_1 C_2 \ddot{V}_O - \frac{C_1 R_2 R_3}{R_4 + R_3} \ddot{V}_O$$

$$- \frac{C_1 R_3 R_2}{R_4 + R_3} \ddot{V}_O$$

-

$$\ddot{V}_O = - \frac{V_I}{A} + \frac{R_1 R_3 C_1}{R_4 + R_3} \frac{1}{A} \ddot{V}_O - \frac{R_1 C_2 R_3}{R_4 + R_3} \frac{1}{A} \ddot{V}_O + \frac{R_1 C_2}{A} \ddot{V}_O$$

$$+ \frac{C_1 R_2 R_3}{R_4 + R_3} \ddot{V}_O + \frac{C_1 R_3 R_2}{R_4 + R_3} \ddot{V}_O$$